

# Tanzil-Lectures

 Search this site

[Course Outline](#)
[Lecture Slides](#)
[Lab Manuals](#)
[MIPS Assembler](#)
[Processor](#)
[Research](#)
[Home](#)

## Current Courses

[CSE 231](#)
[CSE 332](#)
[CSE 499A](#)

## Projects

[CSE332 Project](#)
[CSE231 Project](#)
[CSE 499B](#)
[Thesis](#)

## Teaching Resource

[Course Outline](#)
[Lecture Slides](#)
[Lab Manuals](#)
[Homework](#)
[Exam Question](#)
[Results](#)

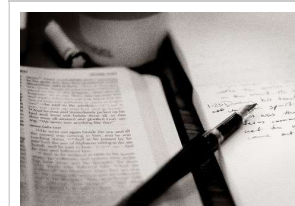
## Previous Courses

[CSE 496](#)
[CSE 331](#)
[CSE3215](#)
[CSE-2214](#)
[CSE-110](#)
[EEE-211](#)
[EEE-212](#)
[EEE-407](#)
[ECO-505](#)
[CSE-211](#)
[CSE3216 Project](#)
[CSE 331 Project](#)

## More Stuff

[Class Announcements](#)
[Office Hours](#)
[Vacancy](#)

## Meet Your Teacher


[Contact Me](#)

## News Link

[Authorship: Who's on first?](#)
[Stupidity in scientific research](#)
[I've taken things,I have a](#)
[passion for](#)
[Stay Hungry,Stay Foolish](#)
[CSE 231 >](#)

## CSE231 Project

### Title : Design Pattern based digital lock system

**Input:** The users will be provided with a keypad for giving input to the system.


**Output :** There will be two types of 7 segments.

7 segment 1: Any input given through keypad will be displayed here.

7 segment 2: If the pattern is correct the result will be displayed in this 7 segment display. Result can be just a letter printed on the 7 segment (O/N).

**Modes:** A user will have two modes to operate the lock. In mode 1, the user can store a specific pattern. In mode 2, user can input a pattern that will be matched with stored pattern. Mode 1 is an advanced requirement and should be attempted only when mode 2 is complete. Mode 2 is the minimum requirement of the project.

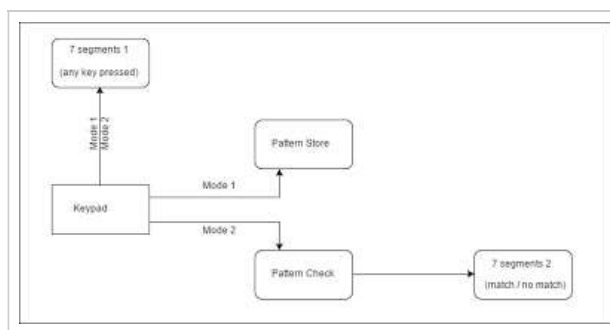**Sample pattern:** The pattern will be fixed for those completing only mode 1. It will consist of the 5 digits in following sequence - sec. no followed by group no and last 3 digits of ID. Say, If you are from Sec 5, Group 4 with an ID 13306996042 the fixed pattern will be 5 4 0 4 2. If different group members have different last 3 digits, you can pick one of them.



Block Diagram of the System

### Submission type:

1. logisim circuit
2. Detail design (pen and paper)
  - a. Specification with blocks
  - b. Truth Table
  - c. Canonical form of functions
  - d. K-map
  - e. simplified function

**Group tasks:** You must list out the name of the members and who has done what part of the project.

### Marks distribution:

- a. Design (Report) – 40
- b. Logisim (Demo)– 30
- c. Viva – 30

### Submission Deadline:

Combinational Part : 20/11/2018 Time : 1.00 - 4.30 PM



**Submit the report at the time of the demonstration**

Sequential Part : 11/12/2018 Time : 1.00 - 4.30 PM

Subpages (1): [CSE 231 \(Project Fall-16\)](#)

**Comments**

You do not have permission to add comments.